 


Sejal M Chopra

4) Instead of minimum mode or maximum mode ,interfacing of any chip (IC-8259,IC-8253,IC-8257 can be asked)

MICROPROCESSOR

Sejal M Chopra



2) Memory Calculations:

EPROM:

Required size = 32 KB, Available size = 16 KB

No. of chips required = Required size / Available size = 2 chips.

No. of sets required = No. of chips required / No. of banks = 2/2 = 1

Set size = Available Chip size x no. of banks = 16 x 2 = 32 KB = $32 \times 1\text{KB} = 2^5 \times 2^{10} = 2^{15}$

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0				7				F				F				F			

Ending Address = FFFFFH

Starting address of EPROM is calculated as:

= Ending Address - Set size

= F F F F F H - 7 F F F F H = F8000H

MICROPROCESSOR

Sejal M Chopra

Chip	Address	Even Bank	Odd Bank
EPROM Set 1	Starting Address	F8000H	F8001H
	Ending Address	FFFFEH	FFFFFH

No. of address lines required for interfacing is dependent on size of a single available EPROM chip

= 16 KB

= $16 \times 1\text{KB} = 2^4 \times 2^{10}$

= 2^{14}

= 14 address lines= (A14 ... A1)...note A0 is reserved for banking....IMPORTANT during interfacing

RAM:

Required size = 128 KB, Available size = 32 KB

No. of chips required = Required size / Available size = 4 chips.

No. of sets required= No. of chips required/ No. of banks= $4/2=2$

Set size= Available Chip size x no .of banks= $32 \times 2 = 64\text{KB}=64 \times 1\text{KB}= 2^6 \times 2^{10}=2^{16}$

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0				F				F				F				F			

Starting address of RAM Set1=**00000H**

Ending address of RAM Set1 is calculated as:

=Starting Address + Set size

=00000 H +0 F F F F H

=**0FFFFH**

Starting address of RAM Set2= Ending address of RAM Set1+1=10000H

Ending address of RAM Set2 is calculated as:

=Starting Address + Set size

=10000 H +0 F F F F H

=**1FFFFH**

Chip	Address	Even Bank	Odd Bank
RAM Set 1	Starting Address	00000H	00001H
	Ending Address	0FFFEH	0FFFFH
RAM Set 2	Starting Address	10000H	10001H
	Ending Address	1FFFEH	1FFFFH

No. of address lines required for interfacing is dependent on size of a single available RAM chip

= 32 KB

= $32 \times 1\text{KB} = 2^5 \times 2^{10}$

= 2^{15}

= 15 address lines

= (A15 ... A1).... note A0 is reserved for banking....IMPORTANT during interfacing

Sejal M Chopra

Let's construct first the memory map

[illegible]

MICROPROCESSOR

Sejal M Chopra

Interpreting Memory Map for Memory Interfacing:

Memory Chip	Address Bus																				Memory Address
	A19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	A0	
RAM 1 (LB)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	00000H
	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	0FFFEH
RAM 2 (HB)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	00001H
	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0FFFFH
RAM 3 (LB)	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	10000H
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1FFFEH
RAM 4 (HB)	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	10001H
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1FFFFH
EPROM 1 (LB)	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	F8000H
	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	FFFFEH
EPROM 2 (HB)	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	F8001H
	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	FFFFFH

Connect these lines on Chips directly

Connect these lines on Chips directly

A18,A17,A16 used for decoding logic

A19 is free line for RAM chips; A19 and A15 are free lines for EPROM chips

A0 line is used for only lower bank


MICROPROCESSOR

Sejal M Chopra

Memory Interfacing:


Step1: Interfacing RAM set1

Memory Chip	Address Bus																				Memory Address
	A19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	A0	
RAM 1 (LB)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	00000H
	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	0FFFFH
RAM 2 (HB)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	00001H
	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0FFFFH

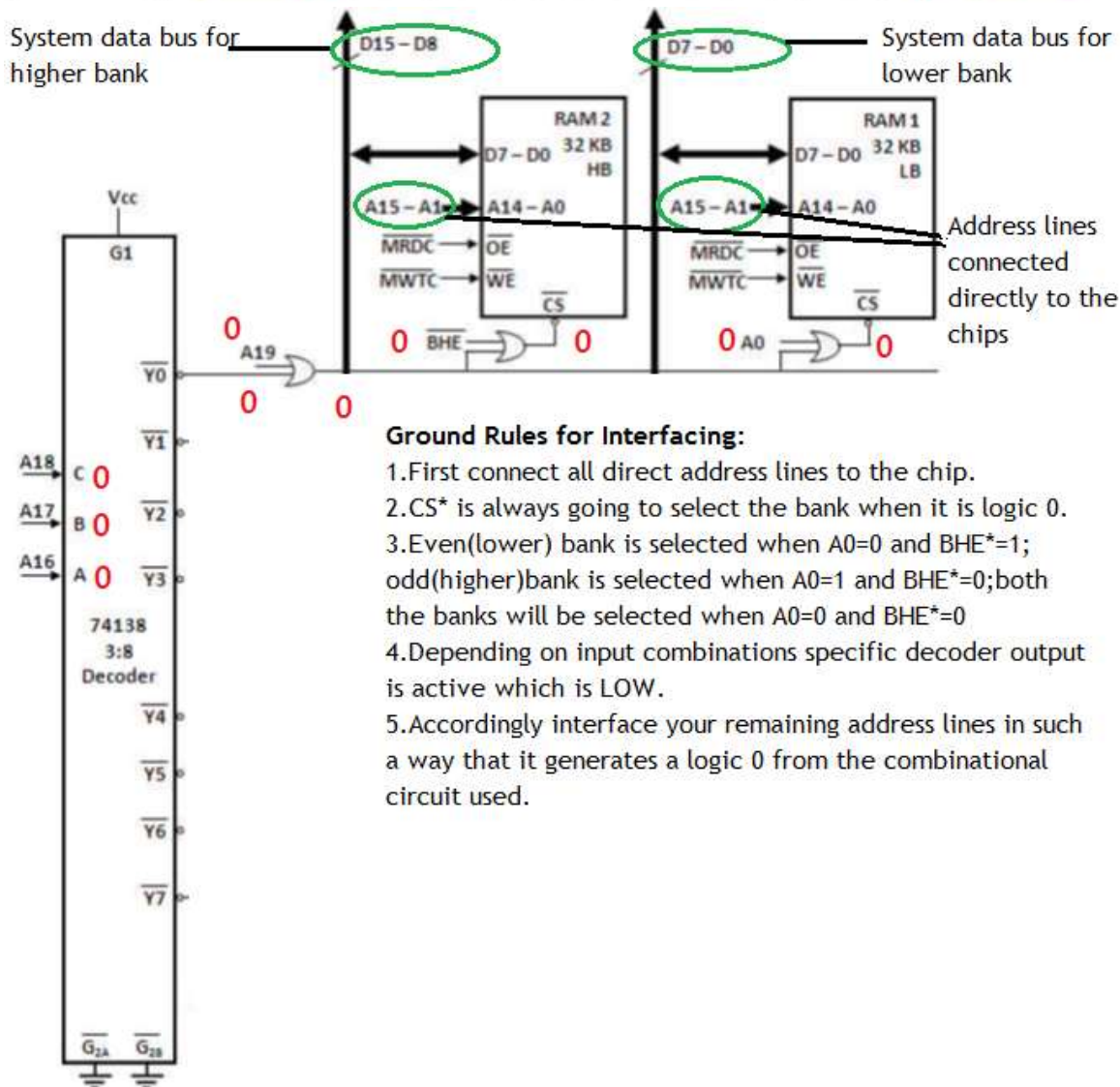


Sejal M Chopra

RAM 3 (LB)	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	10000H 1FFFEH
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	
RAM 4 (HB)	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	10001H 1FFFFH
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	

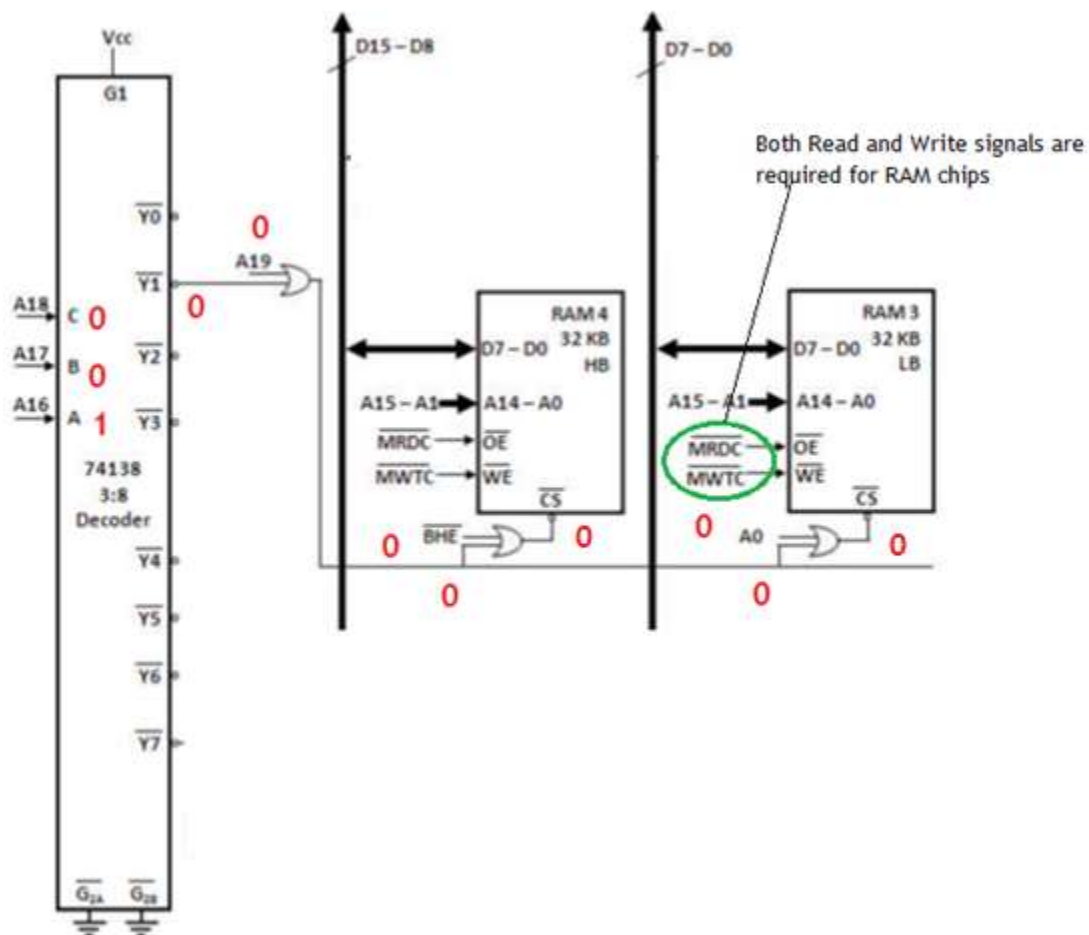

Sejal M Chopra

 [illegible]

- 1) If application memory is mentioned it means RAM chips and if monitor programming memory mentioned it means EPROM chips.
- 2) Generally we use absolute (full) decoding technique (especially block) for memory interfacing.
- 3) Instead of the required size sometimes you have IC numbers given, we need to know their size.

Chips	IC Number	Memory Size(Available Size)
EPROM	2716	2K x 8
	2732	4K x 8
	2764	8K x 8
	27128	16K x 8
	27256	32K x 8
	27512	64K x 8
RAM	6116	2K x 8
	6264	8K x 8
	62256	32K x 8

MICROPROCESSOR

Sejal M Chopra

4) Depending on the address lines used, sometimes we need to use either 2:4 decoder(IC-74139) or 3:8 decoder(IC 74138) or 4:16 decoder(74154)


5) Specifications of these decoders are as follows:

2:4 decoder (IC-74139): It has 2 inputs and 4 active low outputs. It has one active low G_1 pin.

3:8 decoder (IC 74138): It has 3 inputs and 8 active low outputs. It has one active high G_1 pin and two active low G_{2A} and G_{2B} pin.

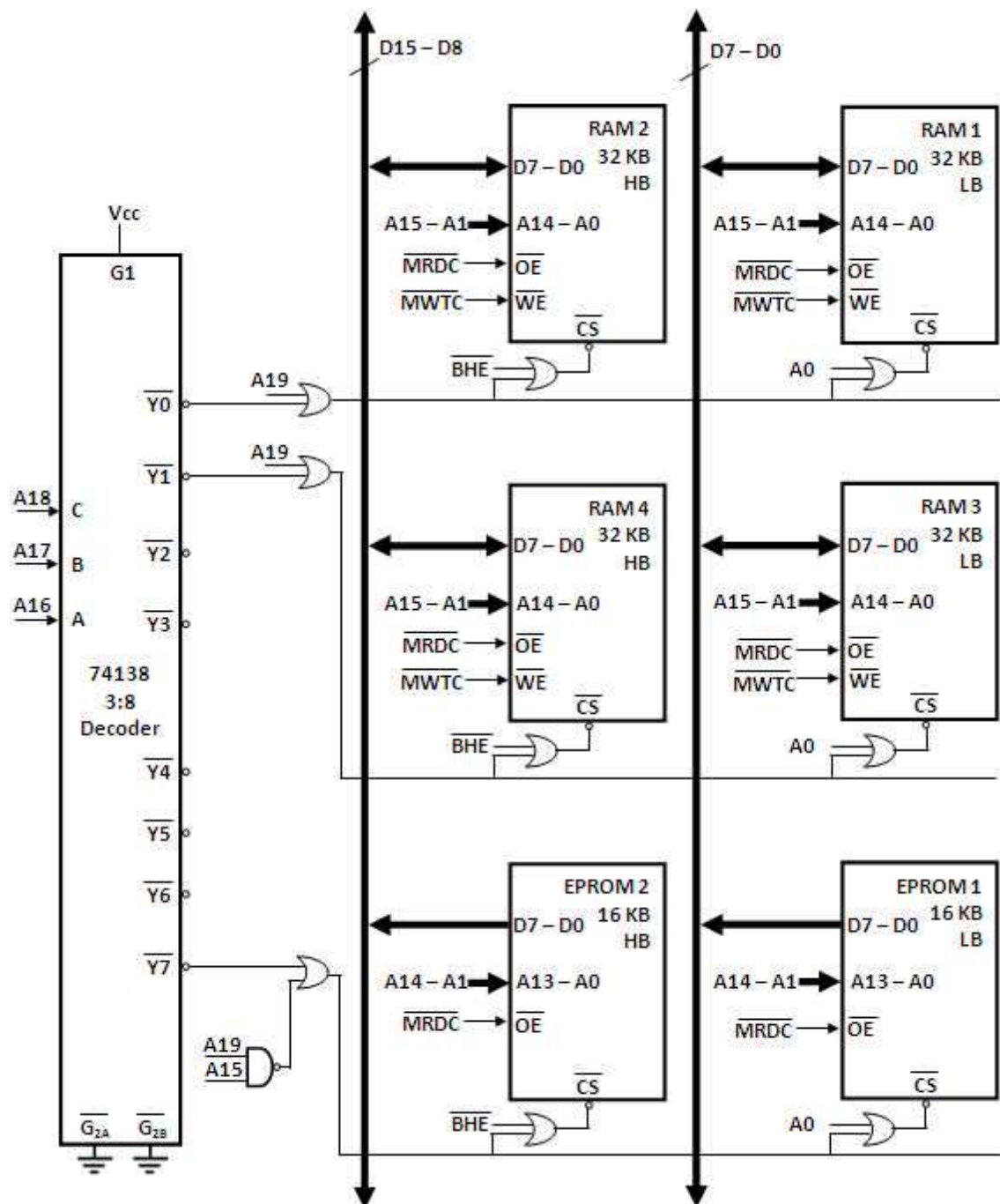4:16 decoder (74154): It has 4 inputs and 16 active low outputs. It has two active low G_1 and G_2 pin.

Complete Interfacing Diagram (You need to draw this final diagram)



MICROPROCESSOR

Sejal M Chopra

IMPORTANT POINTS TO REMEMBER FOR I/O DESIGNING

- Normally I/O devices are mapped using I/O mapped I/O which means I/O devices are given I/O addresses
- Here I/O addresses can be either 8-bit or 16 bit.
- If the question says **direct addressing mode** or **fixed port addressing**, then use an 8-bit address like 80H (A7-A0).
- If the question says **indirect addressing** or **variable port addressing**, then use 16-bit address like 0080H (A15-A0).
- If nothing is mentioned, use **indirect addressing** or **variable port addressing**.
- If memory mapped I/O is asked (Very rare), then remember the following changes
 1. Give the I/O device a 20-bit unused memory address like 80000H (A19-A0)
 2. Connect MEMR* and MEMW* signals to the I/O device instead of the usual IOR* and IOW* signals

I/O Map:

I/O Port	Address Bus																I/O Address
	A15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	A0	
8255 LB																	
Port A	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	0	0060H
Port B	0	0	0	0	0	0	0	0	0	1	1	0	0	0	1	0	0062H
Port C	0	0	0	0	0	0	0	0	0	1	1	0	0	1	0	0	0064H
C Word	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	0	0066H
8255 HB																	
Port A	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	1	0061H
Port B	0	0	0	0	0	0	0	0	0	1	1	0	0	0	1	1	0063H
Port C	0	0	0	0	0	0	0	0	0	1	1	0	0	1	0	1	0065H
C Word	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	1	0067H
8255 LB																	
Port A	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0080H
Port B	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	0082H
Port C	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	0	0084H
C Word	0	0	0	0	0	0	0	0	1	0	0	0	0	1	1	0	0086H
8255 HB																	
Port A	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1	0081H
Port B	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	1	0083H
Port C	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	1	0085H
C Word	0	0	0	0	0	0	0	0	1	0	0	0	0	1	1	1	0087H

Interpreting I/O map for I/O interfacing via 8255IC.

MICROPROCESSOR

Sejal M Chopra

I/O Port	Address Bus																I/O Address
	A15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	A0	
8255 LB																	
Port A	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	0	0060H
Port B	0	0	0	0	0	0	0	0	0	1	1	0	0	0	1	0	0062H
Port C	0	0	0	0	0	0	0	0	0	1	1	0	0	1	0	0	0064H
C Word	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	0	0066H
8255 HB																	
Port A	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	1	0061H
Port B	0	0	0	0	0	0	0	0	0	1	1	0	0	0	1	1	0063H
Port C	0	0	0	0	0	0	0	0	0	1	1	0	0	1	0	1	0065H
C Word	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	1	0067H
8255 LB																	
Port A	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0080H
Port B	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	0082H
Port C	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	0	0084H
C Word	0	0	0	0	0	0	0	0	1	0	0	0	0	1	1	0	0086H
8255 HB																	
Port A	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1	0081H
Port B	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	1	0083H
Port C	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	1	0085H
C Word	0	0	0	0	0	0	0	0	1	0	0	0	0	1	1	1	0087H

Lines A3 -A4 and A8-A15....are all free lines can be utilized in combinational circuit

Used for decoding; output will be on Y3* and Y4*


A0 always reserved for banking

A1 and A2 of processor are connected to A0 and A1 of 8255 and are used for selection of port A,B,C or CWR

MICROPROCESSOR

Sejal M Chopra

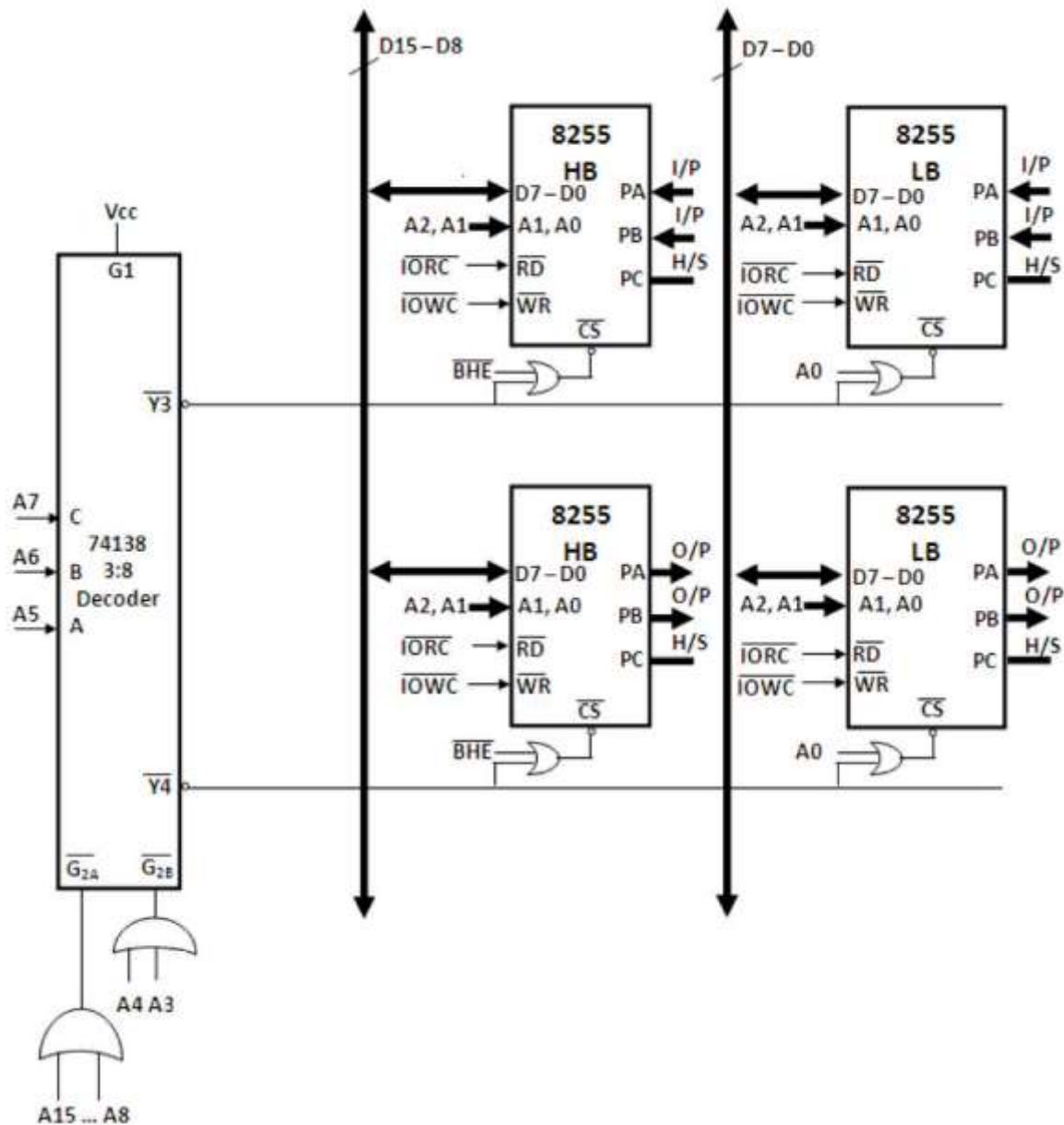Complete Interfacing Diagram (You need to draw this final diagram)



Possible Variations in I/O mapping:

Port Size, quantity and configuration
Two 16-bit input and two 16-bit output ports (Number of 8255 IC's required =4)
One 16-bit input and one 16-bit output port (Number of 8255 IC's required =2)
Two 8-bit input and two 8-bit output ports (Number of 8255 IC's required =2)
One 8-bit input and One 8-bit output port (Number of 8255 IC's required =1)

MICROPROCESSOR

Sejal M Chopra

Practise Question:

Design an 8086 based system working at 7 MHz having the following:

128KB EPROM using 32KB chips,

32KB RAM using 8KB chips,

Two 8-bit input and two 8-bit output ports all interrupt driven

Solution:

Memory Calculations:

EPROM:

Required size = 128 KB, Available size = 32 KB

No. of chips required = Required size / Available size = 4 chips.

No. of sets required = No. of chips required / No. of banks = 4/2 = 2

Set size = Available Chip size x no. of banks = 32 x 2 = 64 KB = 64 x 1KB = $2^6 \times 2^{10} = 2^{16}$

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0				F				F				F				F			

Ending Address of EPROM set1 = FFFFFH

Starting address of EPROM set1 is calculated as:

= Ending Address - Set size

= F F F F F H - F F F F F H = F0000H

Ending Address of EPROM set2 = Starting address of EPROM set1 - 1 = F0000H - 1 = EFFFFH

Starting address of EPROM set2 is calculated as:

= Ending Address - Set size

= E F F F F H - F F F F F H = E0000H

Chip	Address	Even Bank	Odd Bank
EPROM Set 1	Starting Address	F0000H	F0001H
	Ending Address	FFFFEH	FFFFFH
EPROM Set 2	Starting Address	E0000H	E0001H
	Ending Address	EFFFEH	EFFFFH

No. of address lines required for interfacing is dependent on size of a single available EPROM chip = 32 KB

= $32 \times 1\text{KB} = 2^5 \times 2^{10}$

= 2^{15}

= 15 address lines = (A15 ... A1)...note A0 is reserved for banking....IMPORTANT during interfacing

RAM:

Required size = 32 KB, Available size = 8 KB

No. of chips required = Required size / Available size = 4 chips.

No. of sets required = No. of chips required / No. of banks = 4/2 = 2

Set size = Available Chip size x no. of banks = 8 x 2 = 16 KB = 16 x 1KB = $2^4 \times 2^{10} = 2^{14}$

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0				3				F				F				F			

Starting address of RAM Set1 = 00000H

Ending address of RAM Set1 is calculated as:

= Starting Address + Set size

= 00000 H + 0 3 F F F H

= 03FFFH

Starting address of RAM Set2 = Ending address of RAM Set1 + 1 = 04000H

MICROPROCESSOR

Sejal M Chopra

Ending address of RAM Set2 is calculated as:

=Starting Address + Set size

=04000 H +0 3 F F F H

=07FFFH

Chip	Address	Even Bank	Odd Bank
RAM Set 1	Starting Address	00000H	00001H
	Ending Address	03FFE H	03FFF H
RAM Set 2	Starting Address	04000H	04001H
	Ending Address	07FFE H	07FFF H

No. of address lines required for interfacing is dependent on size of a single available RAM chip

= 8 KB

= $8 \times 1 \text{ KB} = 2^3 \times 2^{10}$

= 2^{13}

= 13 address lines

= (A13 ... A1).... note A0 is reserved for banking....IMPORTANT during interfacing

Draw the memory map further for this question and also interfacing diagram.